

## Lab Exercise: 2

### 1. Aim:

To design a simple LED blinking circuit by drawing a circuit diagram and executing it on a breadboard using an Arduino microcontroller.

### 2. Materials Required:

- Arduino Uno
- Breadboard
- LED (any color)
- 220Ω resistor
- Jumper wires
- USB cable for Arduino
- Computer with Arduino IDE installed

### 3. Circuit Diagram:

- Students will first draw a circuit diagram showing the connections between the Arduino, LED, resistor, and ground.
- The positive leg (anode) of the LED is connected to a digital pin (e.g., pin 13) on the Arduino through a 220Ω resistor.
- The negative leg (cathode) of the LED is connected to the ground (GND) of the Arduino.

### 4. Procedure:

#### 1. Draw the Circuit Diagram:

- Use a paper or software like Fritzing/TinkerCAD to create the circuit diagram.

#### 2. Assemble the Circuit on the Breadboard:

- Place the LED on the breadboard.
- Connect the longer leg (anode) of the LED to one end of the 220Ω resistor.
- Connect the other end of the resistor to digital pin 13 of the Arduino.
- Connect the shorter leg (cathode) of the LED to the GND pin of the Arduino.

#### 3. Write and Upload the Code:

- Open the Arduino IDE and write the following code:

```
void setup() {  
    pinMode(13, OUTPUT); // Set pin 13 as an output  
}  
void loop() {  
    digitalWrite(13, HIGH); // Turn the LED on  
    delay(1000); // Wait for one second  
    digitalWrite(13, LOW); // Turn the LED off  
    delay(1000); // Wait for one second  
}
```

**4. Upload the Code to Arduino:**

- Connect the Arduino board to the computer using a USB cable.
- Select the correct board and COM port in Arduino IDE.
- Click on the upload button to transfer the code.

**5. Observe the Output:**

- If the circuit and code are correct, the LED should blink with a 1-second interval.

**5. Expected Output:**

The LED will turn on for one second and turn off for one second repeatedly, indicating that the circuit is functioning correctly.

**6. Conclusion:**

Students successfully designed and implemented a basic IoT circuit for blinking an LED using an Arduino microcontroller. This exercise provides fundamental knowledge of circuit connections and programming in Arduino.